ELEC3441 HW1 PartB Report

Team member:

Name: Bao Xinyang UID: 3035952989 Name: Jiang Feiyu UID: 3035770800


Implementations


All the instructions required, including addi , sw , lw , auipc , beq , bne , blt , bge , jal , jalr are implemented in rv32-full.circ.

Although 3 files are submitted as required, some bugs were found in rv32-full.circ.

When we load the test files to exam the processor, the instruction code sometimes present 0000.... While the instruction still can be processed in the processor.

 e.g. When I load jaljalr.mem into the memory in my computer, the instruction in encoder presents 0000... The result is correct. While when I try it on another classmate's computer, the instruction works correctly.



 

Modifications

- An output pin op1 sel is added to the instruction decoder, as it's required by auipc.
- Only two input pins eq, it is reserved for branch conditions, as they are enough for all branches. The names are changed to avoid confusion with the instruction names.
- A halt is added in B3. When halt is asserted, pc will be reset to 0.

Contribution

The workload of this project is equally distributed.